



The schematic here runs an Atmega328P microprocessor which has components such as bypass capacitors, voltage regulator, servo motor, crystal oscillator, LED, ISP pins, button and a switch. Also components have needed resistors and capacitors.